

First/Second Semester B.E. Degree Examination, June/July 2016

Basic Electronics

Time: 3 hrs.


Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Explain the operation of pn junction diode under forward and reverse bias condition. (06 Marks)
- b. For a zener regulator shown in the Fig.Q.1(b), calculate the range of input voltage for which output will remain constant.

Fig.Q.1(b)

 

$V_z = 6.1V$, $I_{z_{min}} = 2.5 \text{ mA}$, $I_{z_{max}} = 25 \text{ mA}$, $r_z = 0\Omega$.

(04 Marks)

- c. Sketch the transistor input and output characteristics of CE configuration and briefly explain the three regions of operation. (06 Marks)

OR

- 2 a. With circuit diagram, explain the operation of center-tapped full-wave rectifier. Draw input and output waveforms. (06 Marks)
- b. Explain how zener diode can be used as voltage regulator. (05 Marks)
- c. Derive the relationship between α and β . Find the values of β , α and I_E for a transistor has $I_B = 100 \mu A$ and $I_C = 2 \text{ mA}$. (05 Marks)


Module-2

- 3 a. With neat circuit diagram, explain the operation of voltage divider bias circuit with necessary equations. (06 Marks)
- b. Draw the circuit of op-amp integrator. Derive the expression for output voltage. (06 Marks)
- c. Calculate the o/p voltage of a three input inverting summing amplifier, given $R_1 = 200K\Omega$, $R_2 = 250K\Omega$, $R_3 = 500K\Omega$, $R_f = 1M\Omega$, $V_1 = -2V$, $V_2 = -1V$ and $V_3 = +3V$. (04 Marks)

OR

- 4 a. For the circuit shown in Fig.Q.4(a) find the Q-point values and draw DC-load line, where $V_{BE} = 0.7V$ and $\beta = 50$. (06 Marks)

Fig.Q.4(a)

 

- b. Draw the circuit of non-inverting op-amp. Derive the expression for the voltage gain. (05 Marks)
- c. Define the following terms with respect to op-amp: i) slew rate; ii) CMRR; iii) PSRR. (05 Marks)

Module-3

- 5 a. Convert:
- i) $(526.44)_8 = (?)_2 = (?)_{10}$
 - ii) $(48350)_{10} = (?)_{16} = (?)_8$ (04 Marks)
- b. Subtract the following using 2's complement method:
- i) $101011_{(2)}$ from $111001_{(2)}$
 - ii) $111001_{(2)}$ from $101011_{(2)}$ (04 Marks)
- c. Simplify the following expression and realize using basic gates:
 $Y = A(\overline{ABC} + \overline{A}BC)$. (04 Marks)
- d. Realize half adder using NAND gates only. (04 Marks)

OR

- 6 a. Convert:
- i) $(342.56)_{10} = (?)_2 = (?)_8$
 - ii) $(BCDE) = (?)_2 = (?)_8$ (04 Marks)
- b. Perform the subtraction
- i) $(11010)_2 - (10000)_2$ using 1's complement.
 - ii) $(1000100)_2 - (1010100)_2$ using 2's complement. (04 Marks)
- c. State and prove DeMorgan's theorems. (04 Marks)
- d. Write the symbol, truth table and final expression for NAND and Ex – OR gate (For two I/PS). (04 Marks)

Module-4

- 7 a. With diagram and truth table explain NAND gate latch. (05 Marks)
- b. With diagram and truth table explain clocked R-S flip-flop. (05 Marks)
- c. Explain the architecture of 8051 microcontroller. (06 Marks)

OR

- 8 a. What is flip-flop? Explain the operation of NOR gate latch using its truth table. (08 Marks)
- b. With block diagram, explain microcontroller based stepper motor control system. (08 Marks)

Module-5

- 9 a. With the help of block diagram, explain communication system. (06 Marks)
- b. With circuit diagram explain the process of AM demodulation. (05 Marks)
- c. Explain the principle of operation of piezoelectric transducer. (05 Marks)

OR

- 10 a. Why modulation is necessary in communication system? List the different types of modulation schemes. (05 Marks)
- b. A carrier of 1MHz, with 400 W of its power is amplitude modulated with a sinusoidal signal of 2500Hz. The depth of modulation is 75%. Calculate the sideband frequencies, the band width, the power in the side bands and the total power in the modulated wave. (05 Marks)
- c. Explain the construction and the principle of operation of LVDT. (06 Marks)
